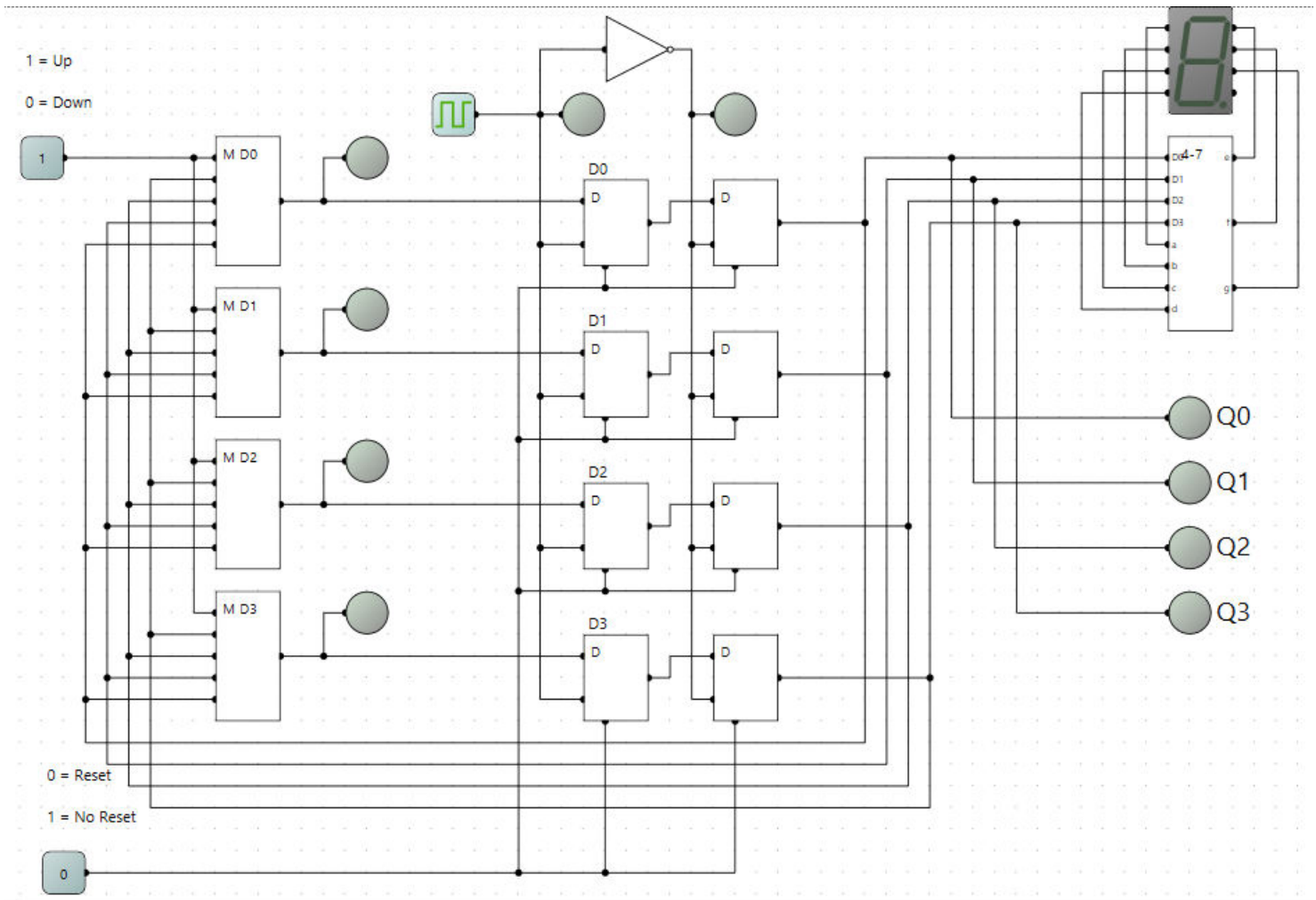












## Lab 4: BCD Up/Down Counter

Alex Weber 817917276

Design: This circuit is designed to print, starting at 0, numbers counting up to 9 or down from 9 depending on the state of the Up/Down bit (0 = Down, 1 = Up). It should also start at 0


### Overall Circuit Schematic:



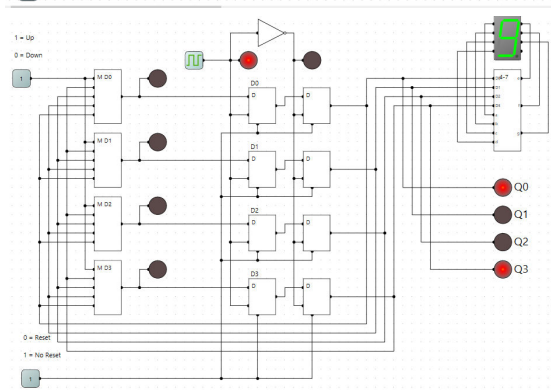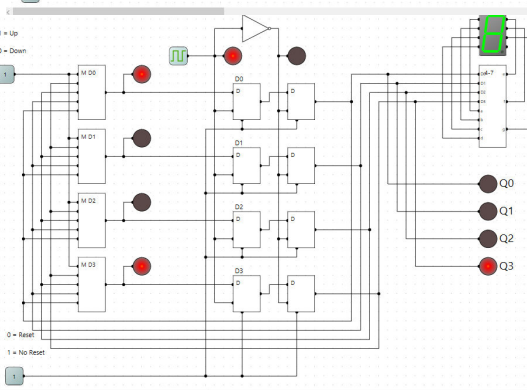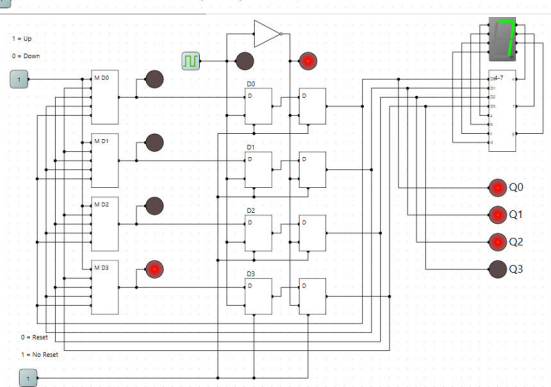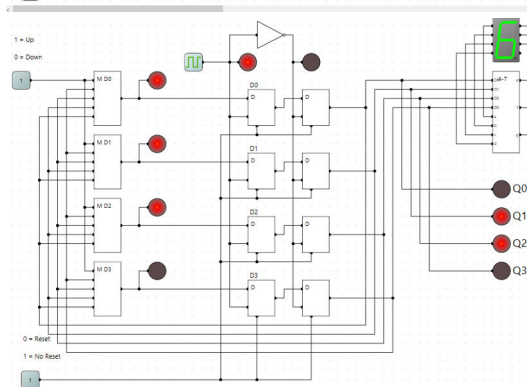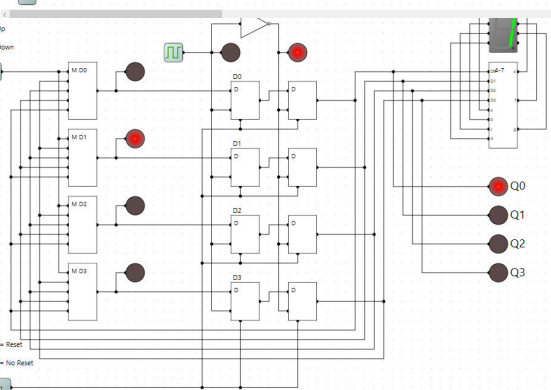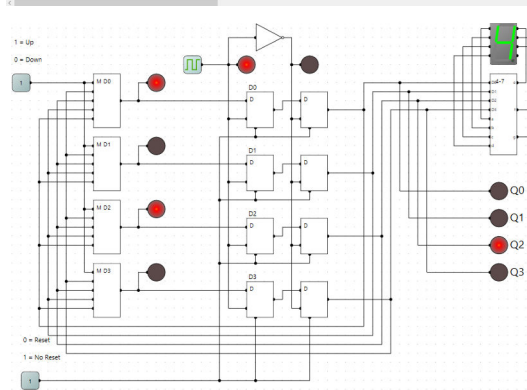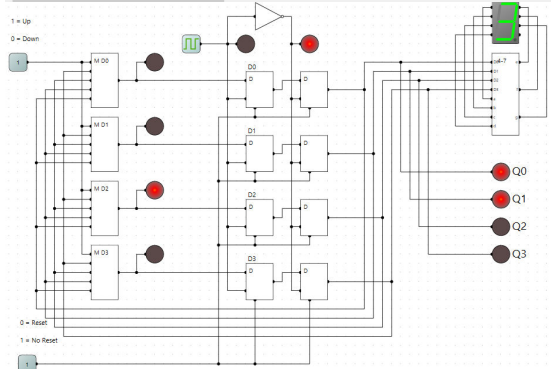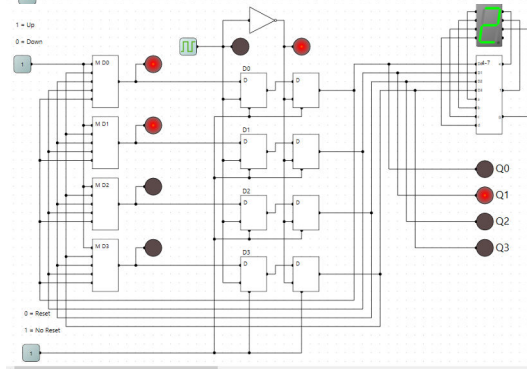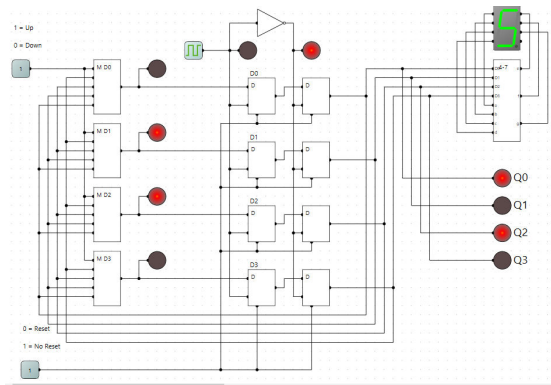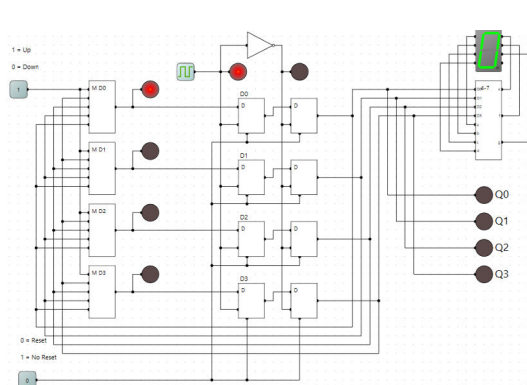





M 0, or Bit 0

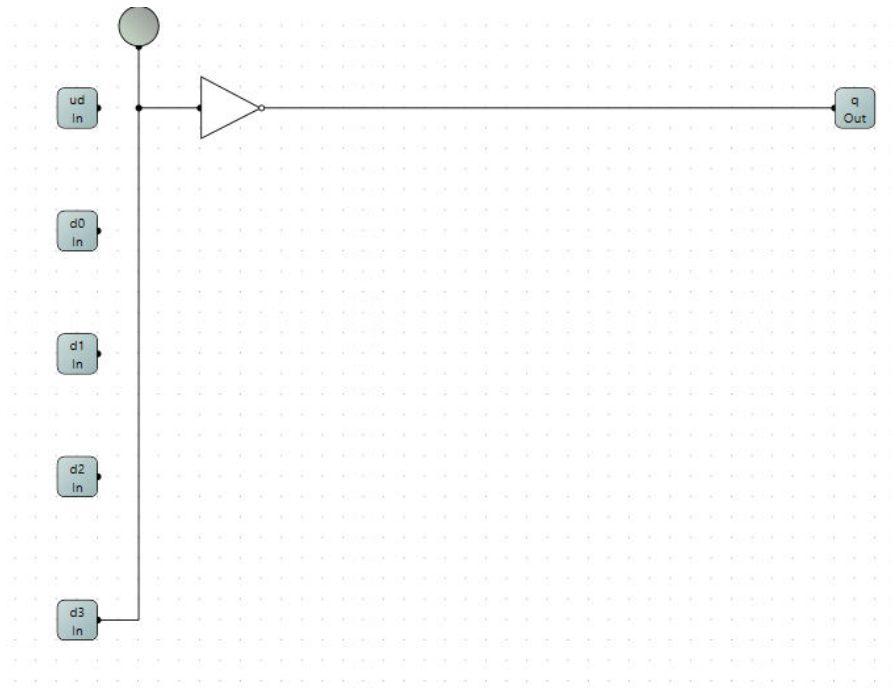


M 1, or Bit 1

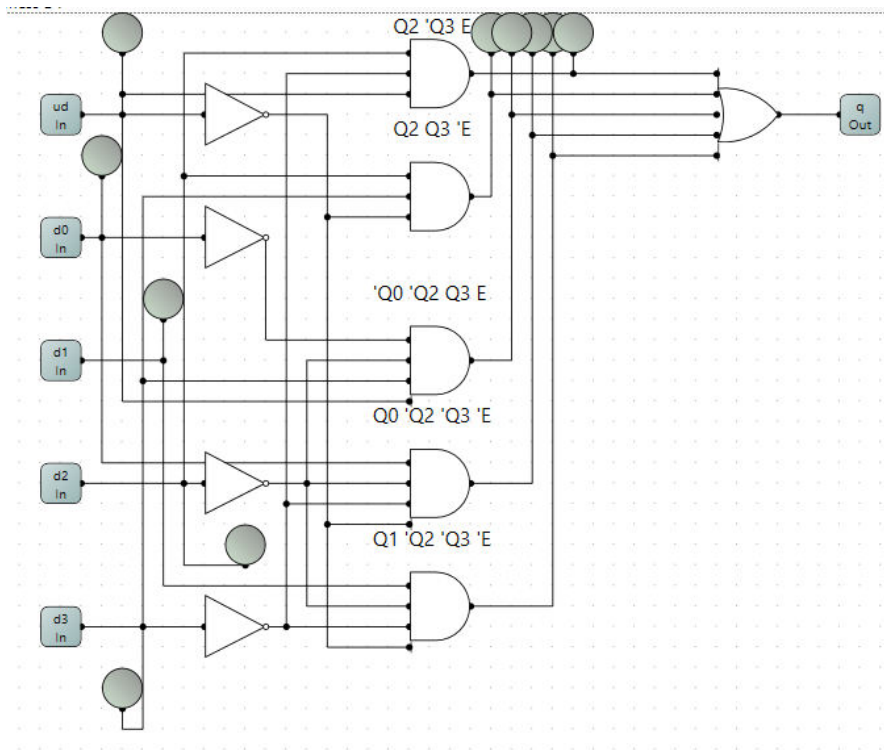


M 2, or Bit 2

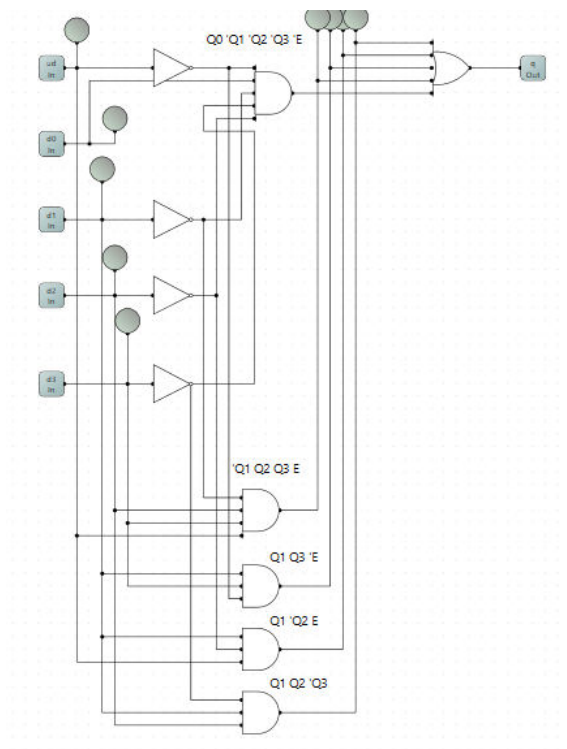

M3 or Bit 3

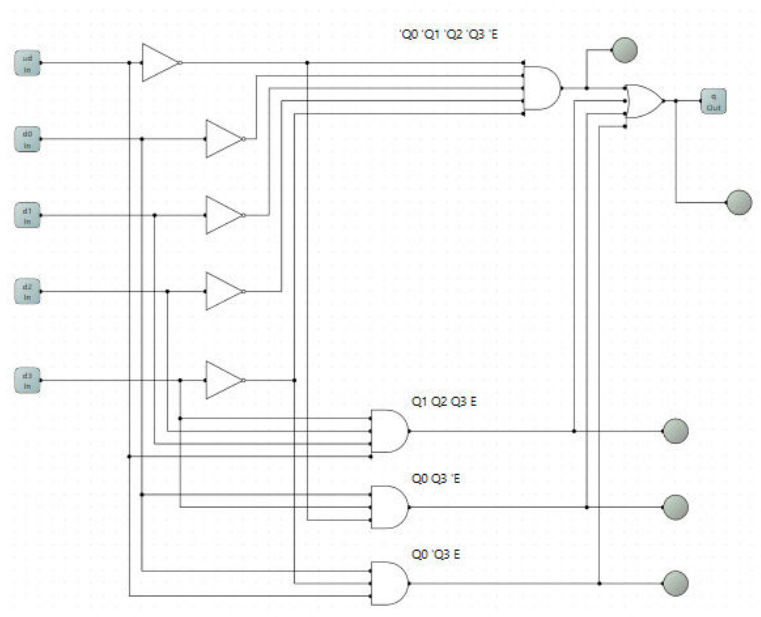

## D-Latch

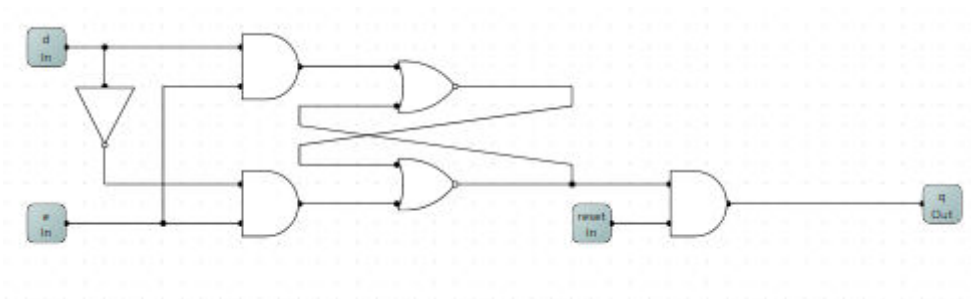


Oscilloscope: For some reason, the Oscilloscope was grayed out no matter whether it was running or not, and with a clock in. I hope the previous pictures provided are enough to show that it works, but I will talk to you today about this.

Video of Up Counter: <http://recordit.co/RhAVVwNG7k>


Video of Down Counter: <http://recordit.co/RVqfb4Ojp2>



## KMap D2

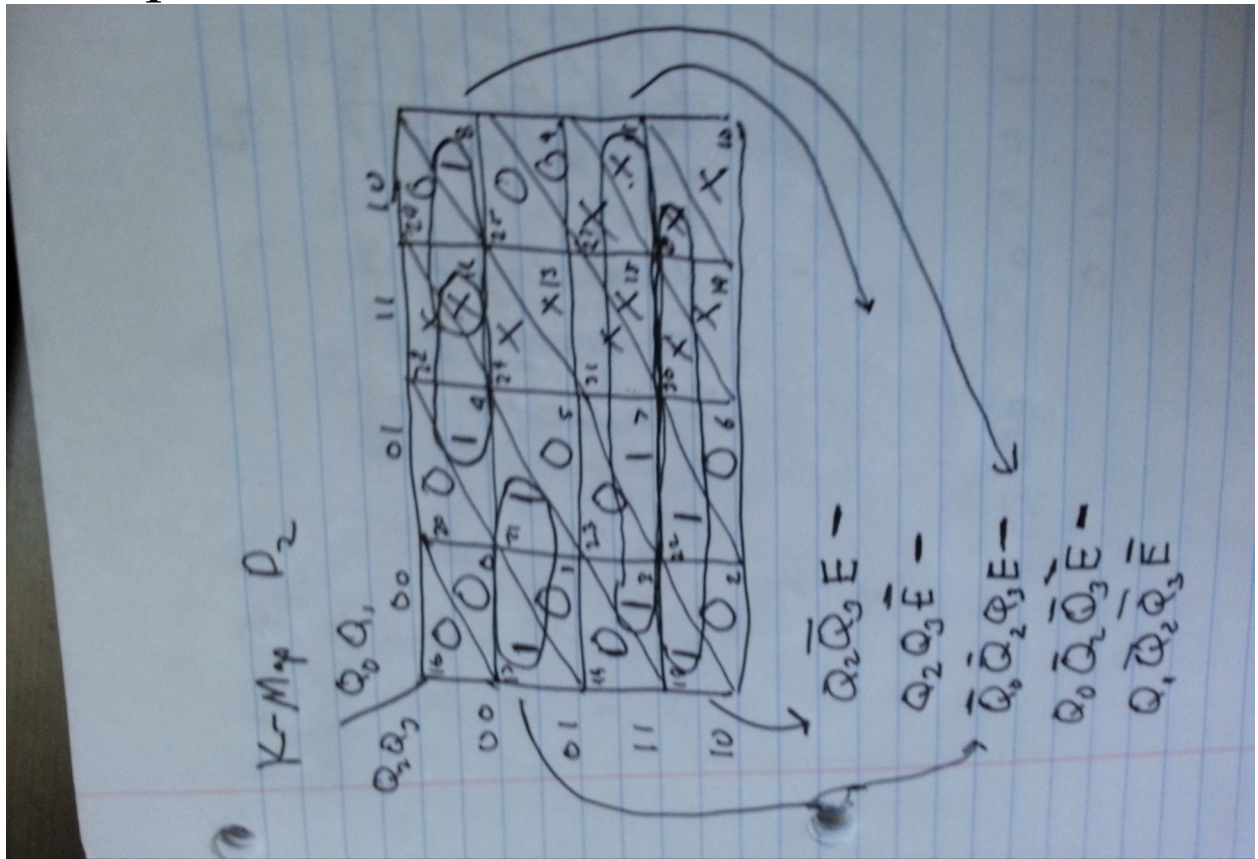


## KMap D3

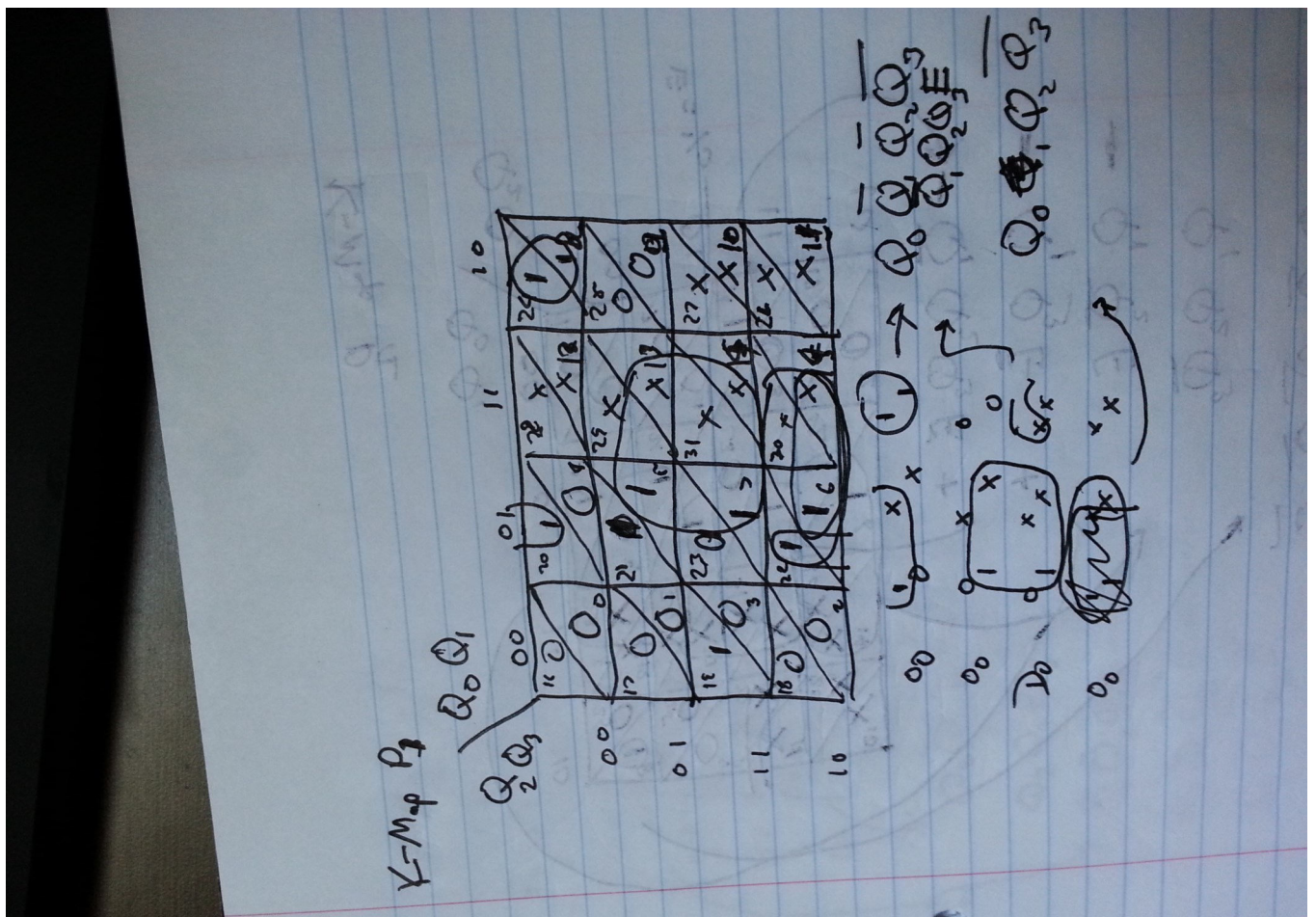




## KMMap D3

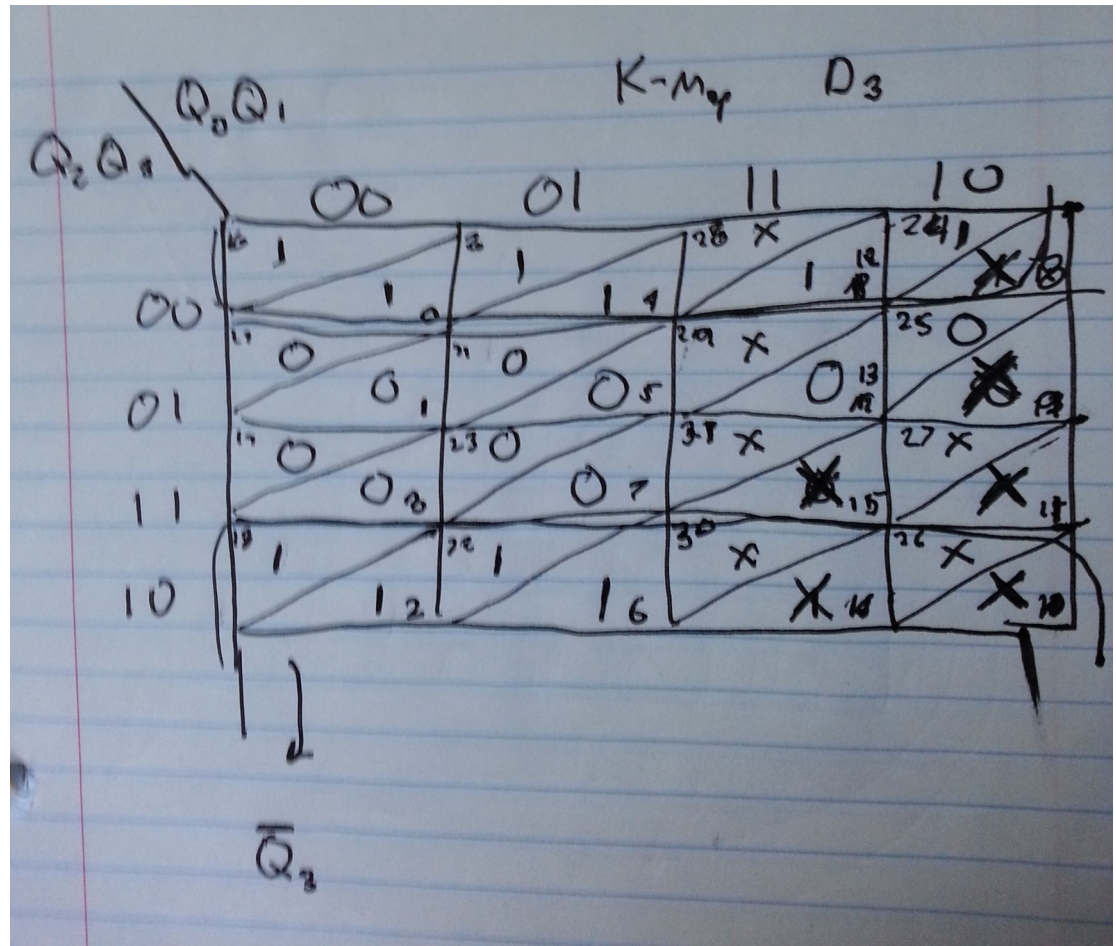

## KMMap D0

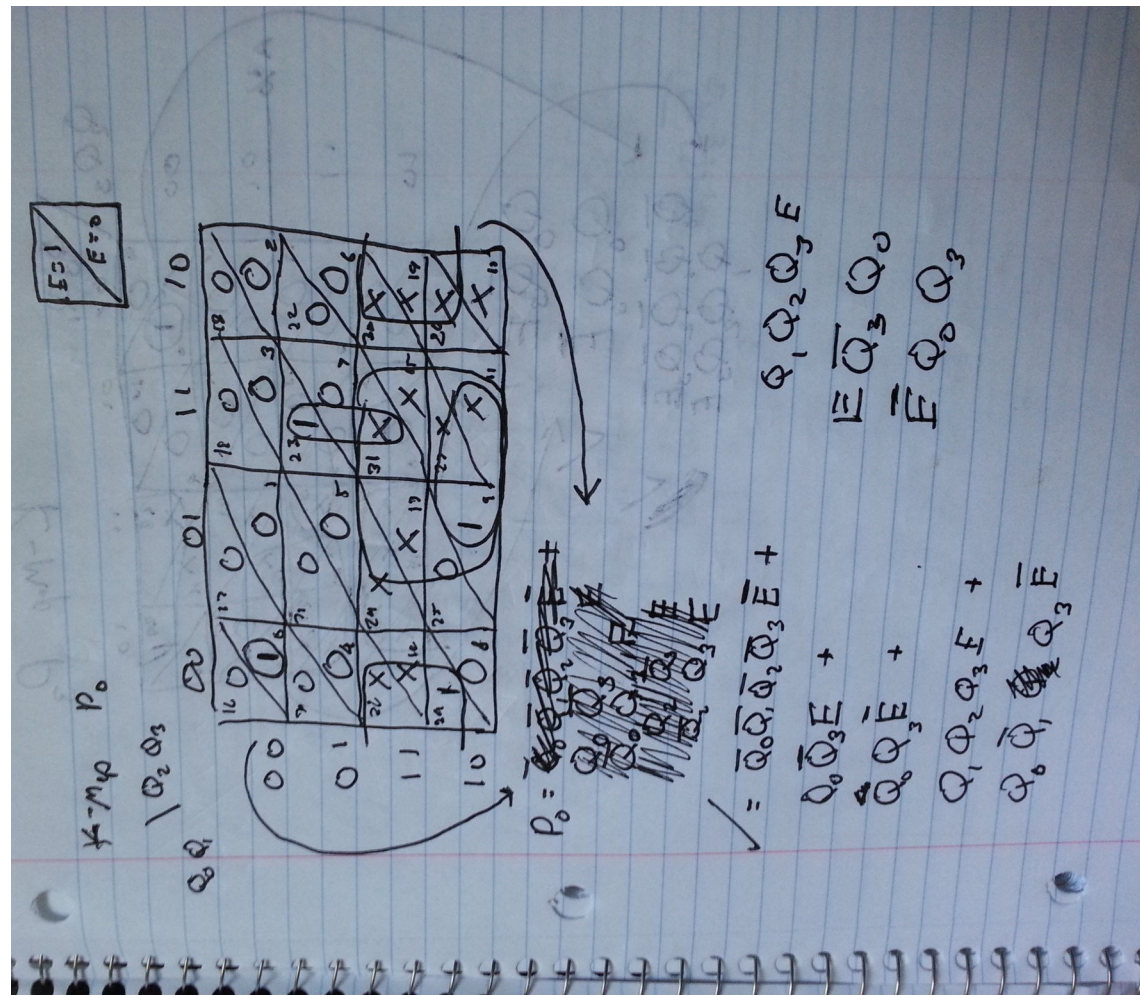



Total

	$Q_0, Q_1, Q_2, Q_3$				#	$Q_0, Q_1, Q_2, Q_3$			
						$E=1$	<del>1000</del>	$E=0$	
$F_0$	0	0	0	0	0	0	0	0	1
$F_1$	0	0	0	1	1	0	0	1	0
$F_2$	0	0	1	0	2	0	0	1	1
$F_3$	0	0	1	1	3	0	1	0	0
$F_4$	0	1	0	0	4	0	1	0	1
$F_5$	0	1	0	1	5	0	1	1	0
$F_6$	0	1	1	0	6	0	1	1	1
$F_7$	0	1	1	1	7	1	0	0	0
$F_8$	1	0	0	0	8	1	0	0	1
$F_9$	1	0	0	1	9	0	0	0	0

