

Lab 4: BCD Up/Down Counter Alex Weber 817917276


Design: This circuit was designed to print my modified RedID (817917256, replacing the 7 at the end with a 5 in order to make this project feasible) forward using finite state machines and latches. I did the extra credit, letting it count up or down.

Overall Circuit Schematic:

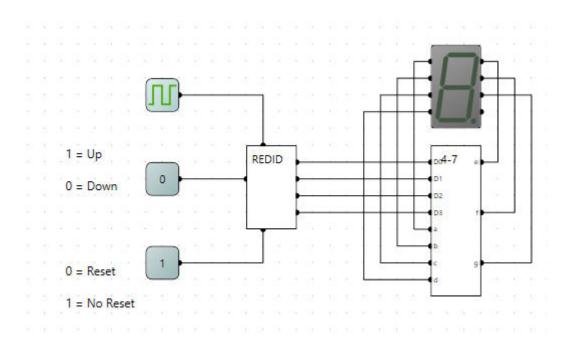


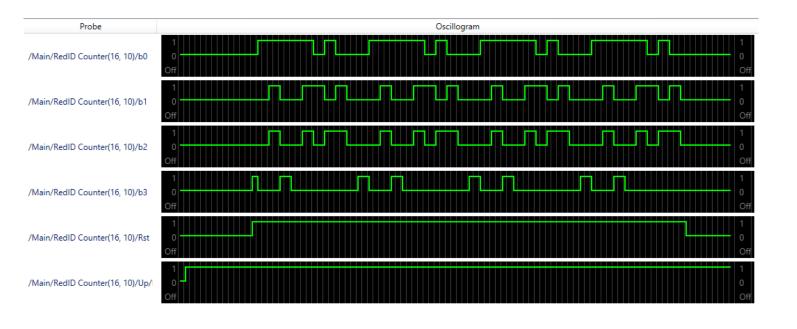Oscilloscope for counting in BCD up and BCD down




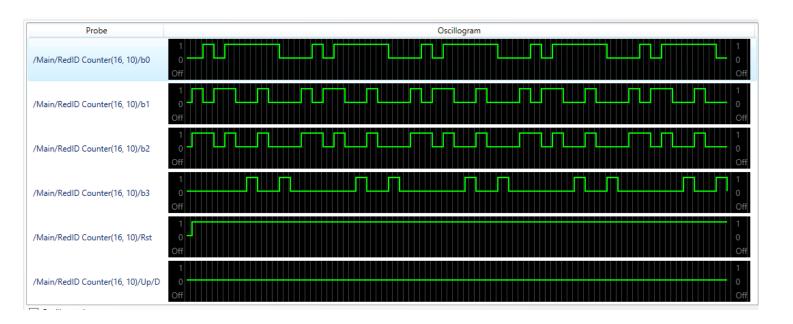


M 0, or Bit 0

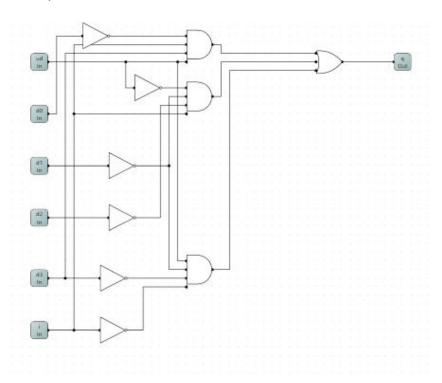

M 1, or Bit 1

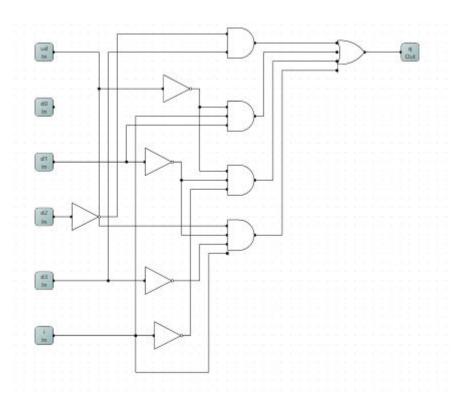


M 2, or Bit 2

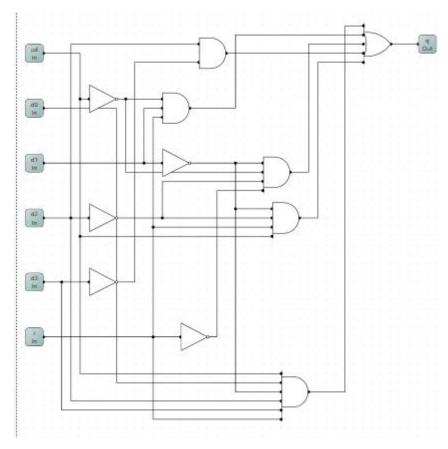


M3 or Bit 3


D-Latch

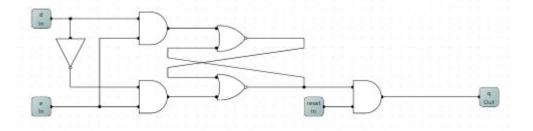

Indicator Logic

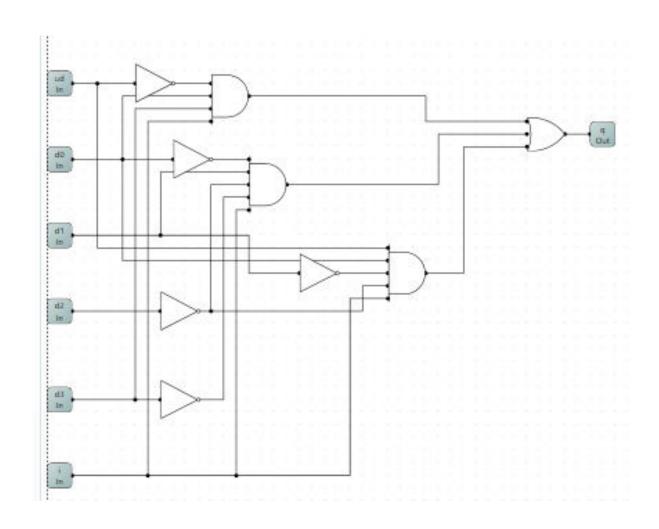


Overall Circuit Diagram

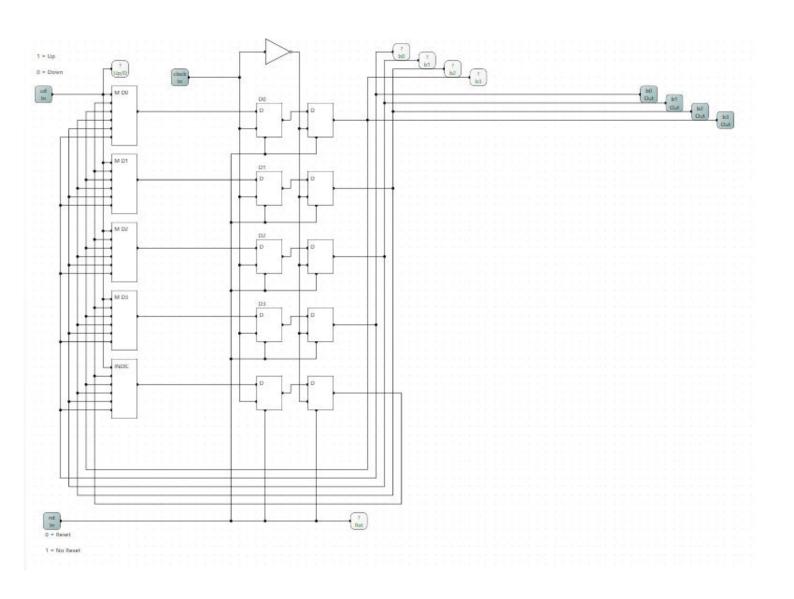


'Master' Truth Table

0	0	0	0	0	0	0	0 0->6	0->8		0	1	1	0
1	0	0	0	0	0	1	8 8->0	8-51	_	1	0	0	1
									_				
2	0	0	0	0	1	0	1 1-> 8	1->7		0	1	1	1
3	0	0	0	0	1	1	7 7->1	7->9	- X	8	8	8	8
4	0	0	0	1	0	0	9 9->7	9 -> 1	8	8	8	8	8
5	0	0	0	1	0	- 1	1 1-> 9	1->7		0	0	1	0
6	0	Ö	0	1	1	0	7 7->1	7->2	_	0	1	0	1
									_				
7	0	0	0	1	1	1	2 2->7	2->5		0	0	0	1
8	0	0	1	0	0	0	5 5->2	5 -> 6		0	0	0	0
9	0	0	1	0	0	- 1	6 6-55	6 -> 0		0	1	1	1
10	0	0	1	0	1	0	AX	8	8	8	8	8	8
11	0	0	1	0	1	1	BX	8	8	X	8	X	×
12	0	0	1	1	0	0	CX	8	8	8	8	8	8
13	0	0	1	1	0	- 1	D X	8	8	8	8	8	8
14	0	0	1	1	1	0	E X	8	8	8	8	8	8
15	0	0	1	1	1	1	F X	8	8	8	8	8	8
16	0	1	0	0	0	0	0			0	1	1	0
17	0	1	0	0	0	- 1	1			1	0	0	0
18	0	1	0	Ö	1	0	2			0	1	1	1
19	0	1	0	0	1	1	3		X	8	8	8	8
20	0	1	0	1	0	0	4		X X	8	8	8	8
21	0	1	0	1	0	1	5			0	0	1	0
22	0	1	0	1	1	0	6			0	1	0	1
23	0	1	0	1	1		7			0	0	0	1
24	0	1	1	0	0	0	8			0	0	0	0
25	0	1	1	0	0	1	9			0	1	1	1
26	0	1	1	0	1	0	A 8	8	X	8	8	8	8
27				0		1	BX						
	0	1	1		1			8	8	8	8	8	8
28	0	1	1	1	0	0	CX	8	8	8	8	8	8
29	0	1	1	1	0	1	D X	8	8	8	8	8	8
30	0	1	1	1	1	0	E X	8	8	8	8	8	8
31	0	1	1	i	1	Ť	F X	8	8	8	8	8	8
32	1	0	0	0	0	0	0	0->8		1	0	0	0
33	1	0	0	0	0	1	8	8-51		0	1	1	1
34	1	0	0	0	1	0	1	1->7		0	1	0	1
35	1	0	0	0	1	1	7	7->9	8	8	8	8	8
36	1	0	0	1	0	0	9	9->1	X	X	8	X	8
37	1	0	0	1	0	1	1	1->7		0	1	1	0
38	1	0	0	1	1	0	7	7->2		0	0	0	0
39	1	0	0	1	1	1	2	2->5		1	0	0	1
40	1	0	1	0	0	0	5	5->6		0	0	0	1
41	1	0	1	0	0	1	6	6 -> 0		0	0	0	1
42	1	0	1	0	1	0	A X	8	8	8	8	8	8
43	1	0	1	0	1	- 1	BX	8	8	8	8	8	8
44	1	0	1	1	0	0	C X	8	8	8	8	8	8
45	1	0	1	1	0	1	DX	8	8	8	8	8	8
46	1	0	1	1	1	0	E X	8	8	8	8	8	8
47	1	0	1	1	1	- 1	F X	8	8	8	8	8	8
	1	1	0	0	Ö	Ö	0			1	0		0
48												0	
49	1	1	0	0	0	1	1			0	1	1	1
50	1	1	0	0	1	0	2			0	1	0	1
51	1	1	0	0	1	- 1	3		8	8	8	8	8
52	1	1	0	1	0	0	4		8	8	ä	8	8
53	1	1	0	1	0	1	5			0	1	1	0
54	1	1	0	1	1	0	6			0	0	0	0
55	1	1	0	1	1	1	7			0	0	1	0
56	1	1	1	0	0	0	8			0	0	0	1
57	1	1	1	0	0	1	9			0	0	0	1
	1	1	1	0	1	0	AX	8	8	X	8	8	8
58	• 1												
58		1	- 1	0	1	1	BX	- X	X X	X	X	X	X
	1	1	1	1	0	1	B X C X	X X	8 8	8 8	8 8	8 8	8 8


KMap D0

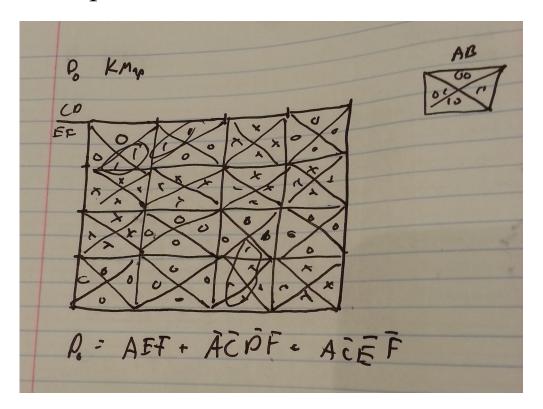


KMap D1

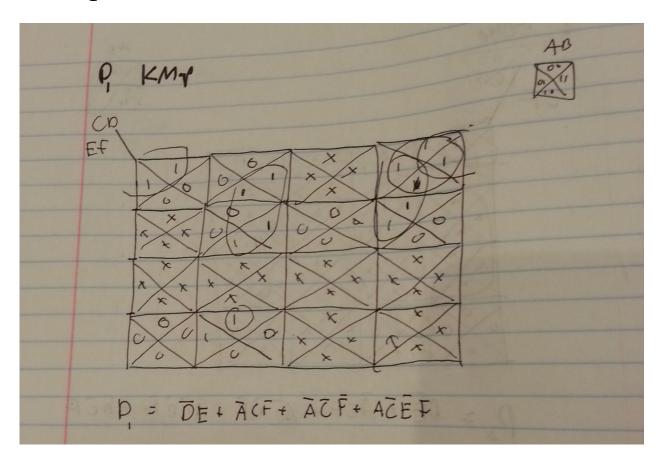


KMap D2

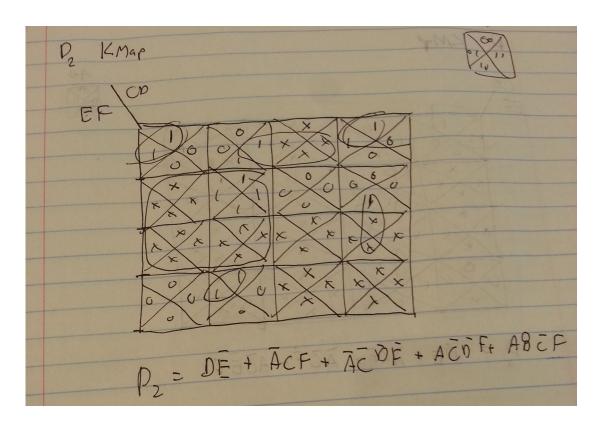

KMap D3

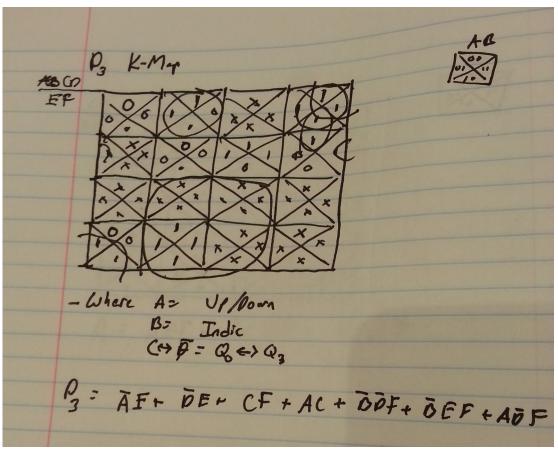

Indic KMap

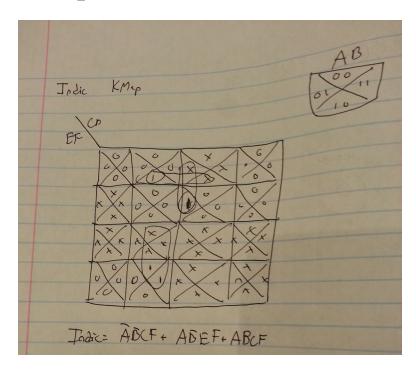

FSM

